




PWM呼吸燈

國立成功大學 電機系
2022

呼吸燈

1. 白光呼吸燈
2. 混色光呼吸燈

 

目錄

-
- 紅 Red
- 洋紅 Magenta
- 黃 Yellow
- 白 White
- 藍 Blue
- 青 Cyan
- 綠 Green



Duty cycle

50% duty cycle



75% duty cycle



25% duty cycle




$$Duty = \frac{T_{ON}}{Period\ T}$$

Pulse Wave

- Pulse-wave Modulation (PWM) Uses a rectangular pulse wave whose pulse width is modulated resulting in the variation of the average value of the waveform.
- Average value of a pulse waveform $f(t)$ with period T and low value V_L high V_H can be found as

$$\bar{y} = \frac{1}{T} \int_0^T f(t) dt$$

 
$$V_{avg} = D \cdot V_H + (1 - D) \cdot V_L$$




- In general V_L is zero; D is the duty; $V_{avg} = D \times V_H$
- The average value of the signal is directly dependent on the duty cycle D .
- Output signal alternates between on and off within a specified period.

Lead Edge Modulation


Modulation Wave

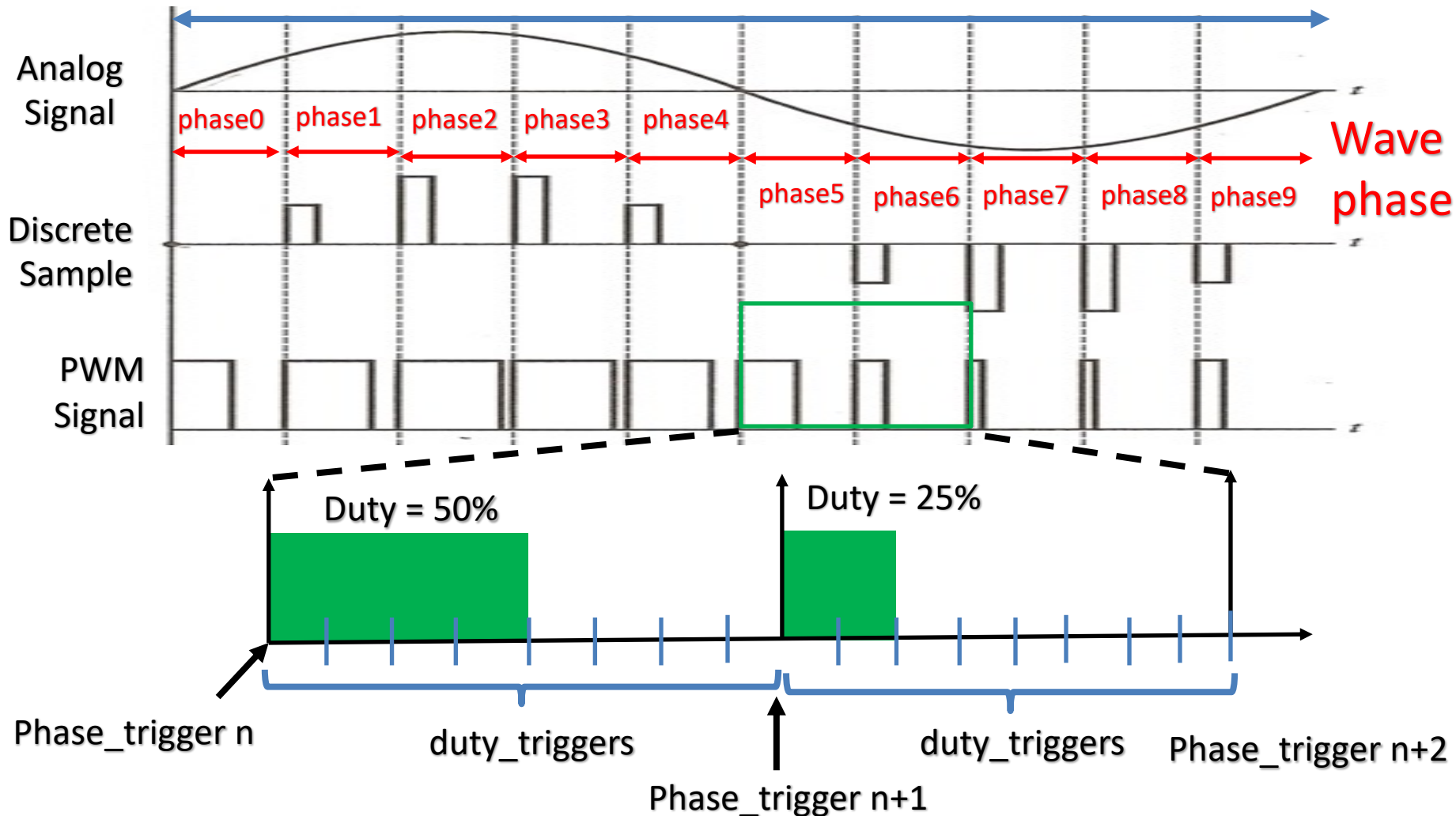


Simple Lead Edge Modulation

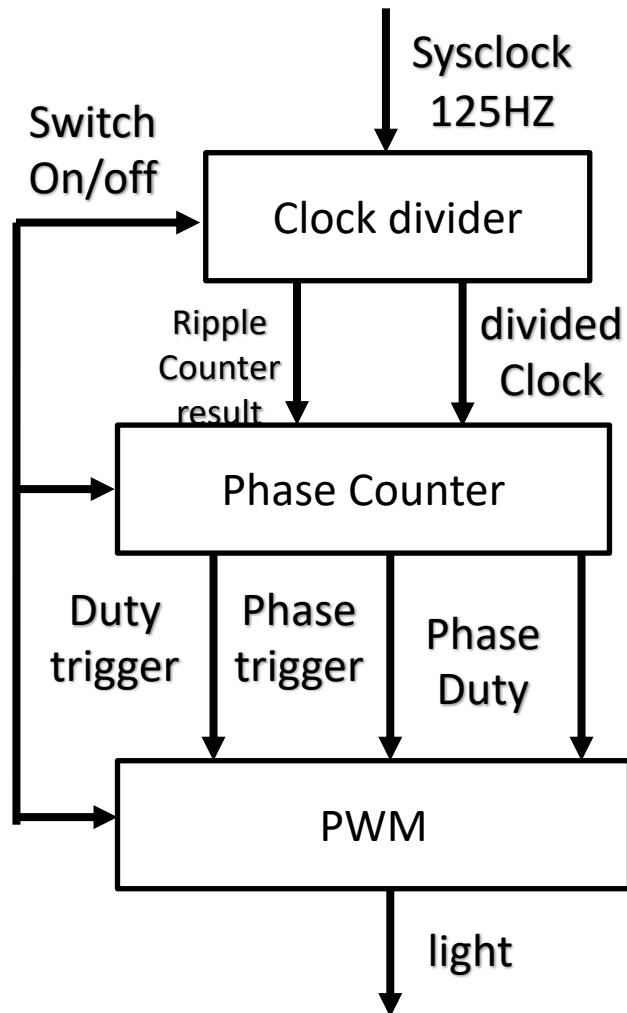

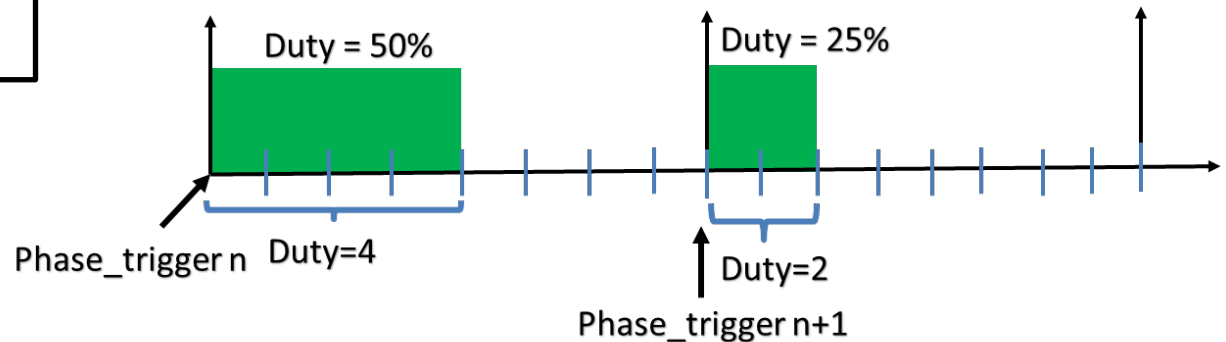- 由於125MHZ的Sysclk頻率太高，請嘗試以 Clock Divider 將頻率降至適合操作的頻率。
(Hint : divided clock frequency = $\frac{125\text{MHZ}}{2^n}$)
- 當Phase trigger的週期小於眼睛圖像滯留時間(約為40ms)，可減少目視閃爍的現象。
- Phase trigger週期須為Duty trigger週期的倍數。
- Duty 為每次phase trigger後維持高位的cycle
假設Phase trigger週期為8 cycle, phase duty = 4 cycle
那PWM的 Duty = 50%。




Clock Divider

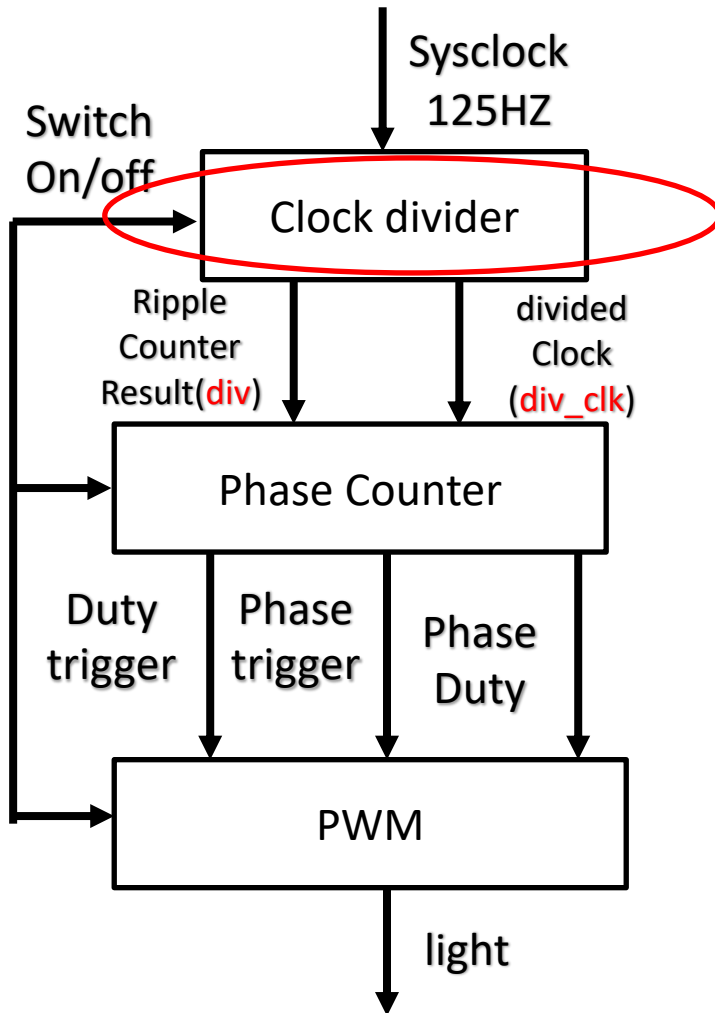

```
module ripple_div(  
    input rst,  
    input sysclk,  
    output wire [31:0] div,  
    output wire div_clk  
);  
//31  
dff_div d0( .rst(rst), .trigger(sysclk), .div(div[0]));  
dff_div d1( .rst(rst), .trigger(div[0]), .div(div[1]));  
...  
...  
...  
dff_div d31( .rst(rst), .trigger(div[30]), .div(div[31]));  
endmodule
```


Phase Counter

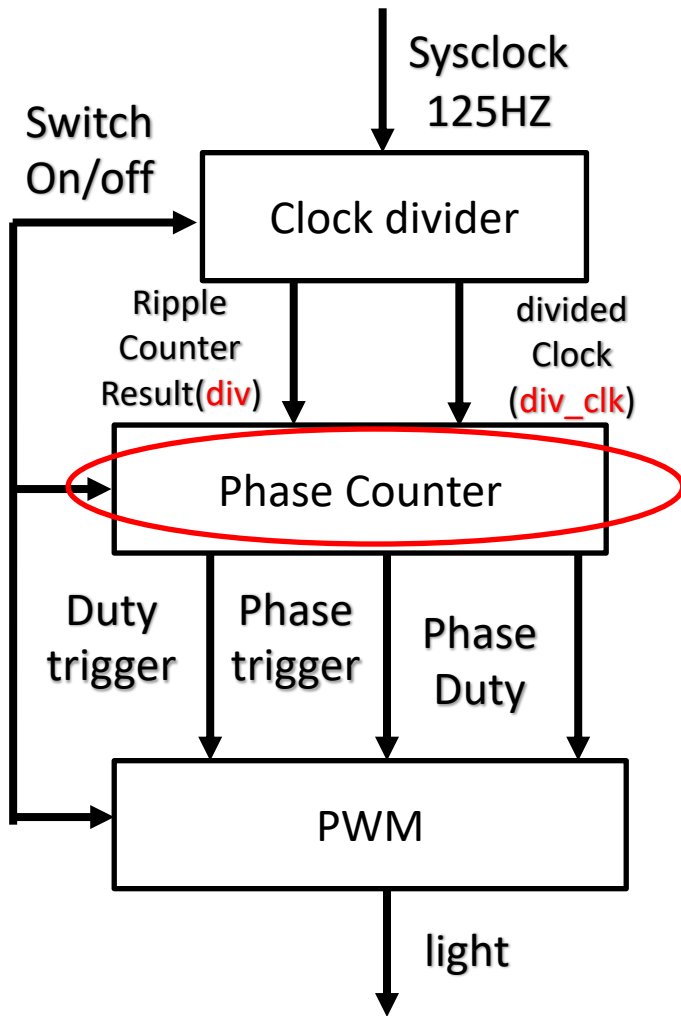


```
module phase_counter(  
    input rst,  
    input enable,  
    input [7:0] phase_shift,  
    input[31:0] div,  
    input div_clk,  
    output wire duty_trig,  
    output wire phase_trig,  
    output wire [7:0] phase  
);
```

```
reg [7:0] duty;  
assign duty_trig = (div[7:0] == 8'hff) & enable;  
assign phase_trig = (div[15:0] == 16'hff) & enable;  
assign phase     = div[27:20] + phase_shift;  
  
endmodule
```

8 bit phase

PWM

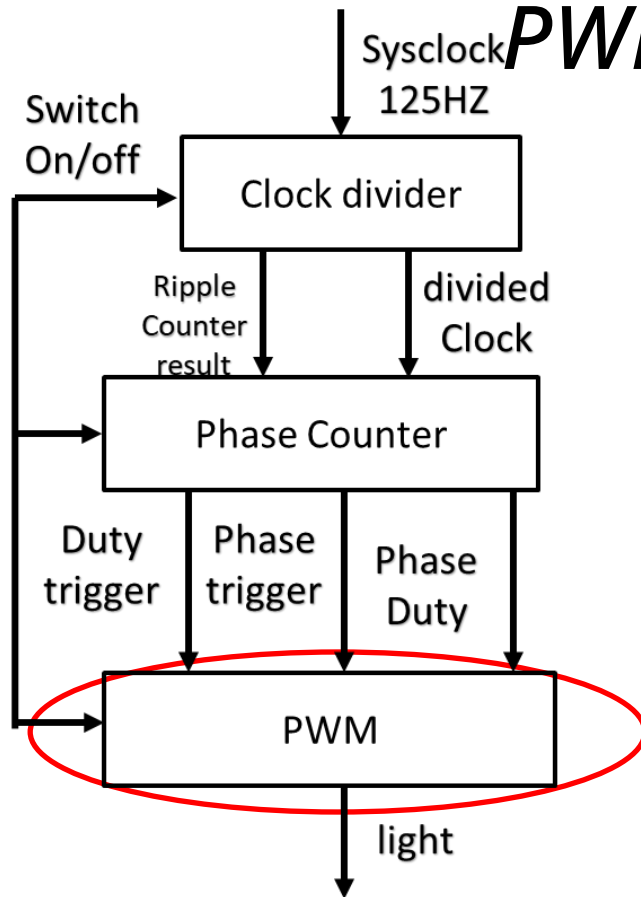


*256 duty cycles between
Phase_triggers*


```

module pwm(
    input rst,
    input enable,
    input duty_trig,
    input phase_trig,
    input [7:0] phase,
    output wire out
);
reg[7:0] count;
assign out = ((count < phase) | phase_trig) & enable;
always@(posedge duty_trig or posedge rst)begin
    if(rst)begin
        count <= 8'b0;
    end else if(phase_trig)begin
        count <= 8'b0;
    end else if(duty_trig)begin
        count <= count + 1;
    end else begin
        count <= count;
    end
end
endmodule
  
```

Clock Divider1

 


Divide clock frequency by 2

 

```
module dff_div(  
    input n_rst,  
    input trigger,  
    output reg div  
);  
  
always @(posedge trigger or negedge n_rst)begin  
    if(!n_rst)begin  
        div <= 1'b0;  
    end else begin  
        div <= !div;  
    end  
end  
endmodule
```

Clock Divider2

Clock divide by 2^n (n DFF個數)

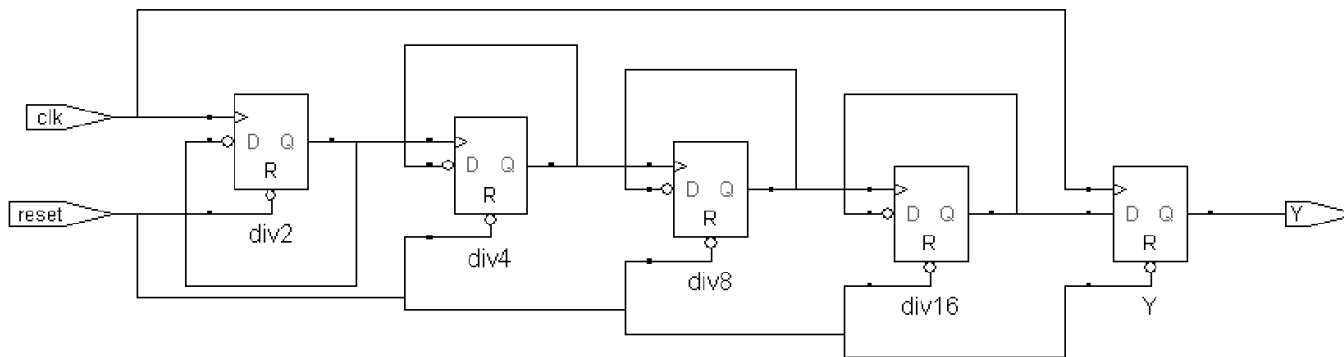


Divided clock frequency


$$\text{freqY} = \frac{125\text{MHZ}}{2^n}$$

($n=\text{\#DFF}$)


Name	Value
sysclk	1
div2	1
div4	1
div8	1
div16	0
Y	0

 


Ripple Counter

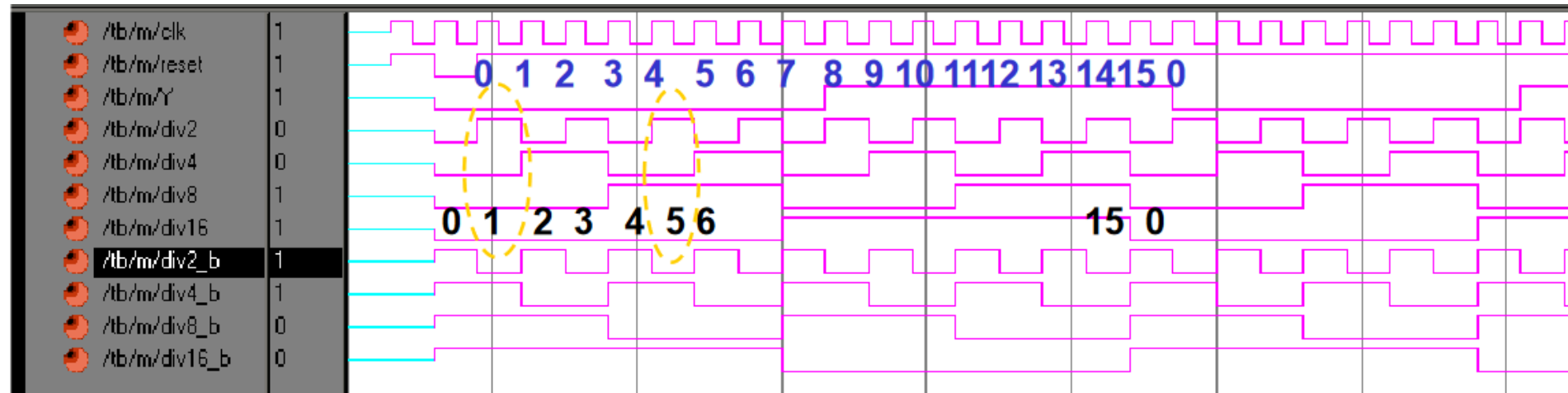

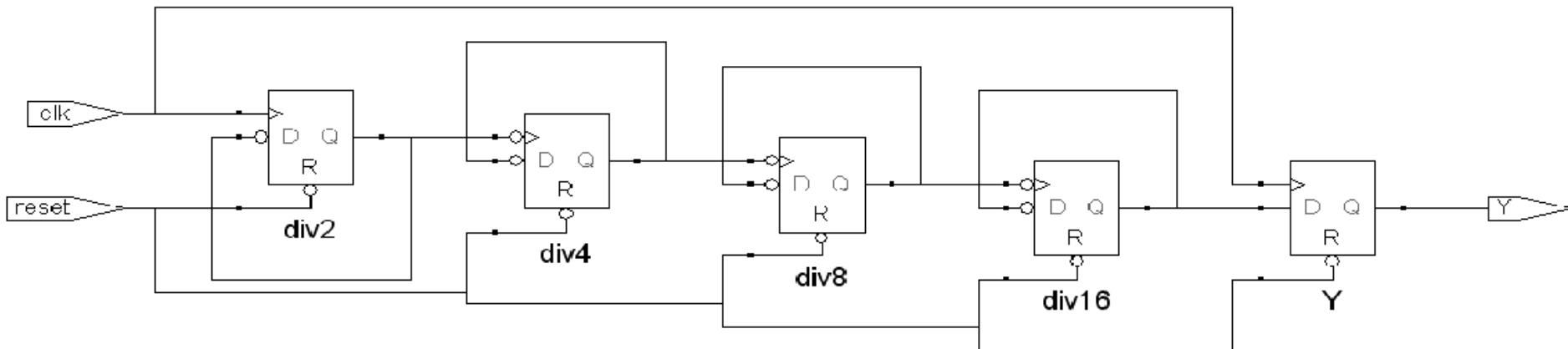Count-up counter $0 \rightarrow 1 \rightarrow 2 \rightarrow \dots \rightarrow 15 \rightarrow 0 \rightarrow 1 \rightarrow 2 \rightarrow \dots$



Synchronous counter

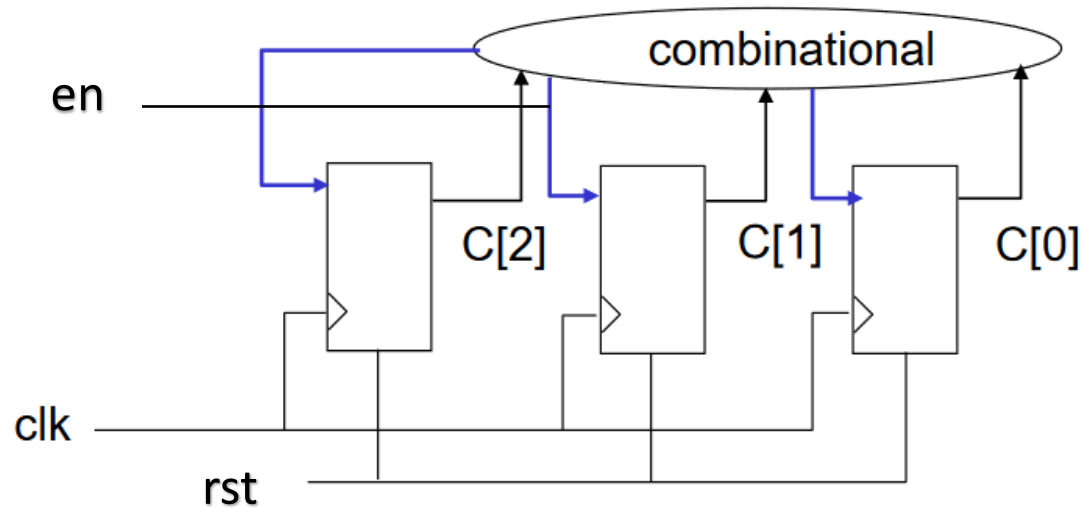

C(old)	C(new)
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	0 1 1
...	
1 1 0	1 1 1
1 1 1	0 0 0

```
always@(posedge clk or posedge rst)begin
  if(rst)begin
    C <= 3'b0;
  end else if(en)begin
    C <= C + 3'b1;
  end else begin
    C <= C;
  end
end
```

Digital Sinusoidal wave

/*NOTE

LUT_sin table is a wave look up table with 8 bit
index from 0~255



the range of output data 0 ~ 255

*/

```
) module LUT_sin(  
    input[7:0] phase_idx,  
    output reg[7:0] data  
);
```



Simulation

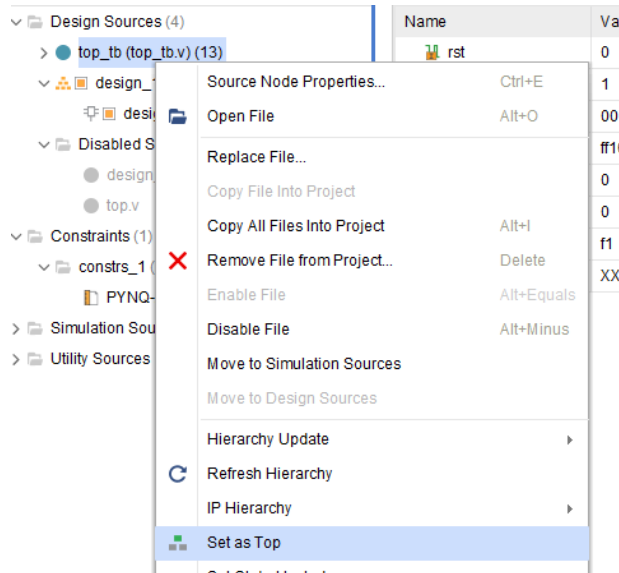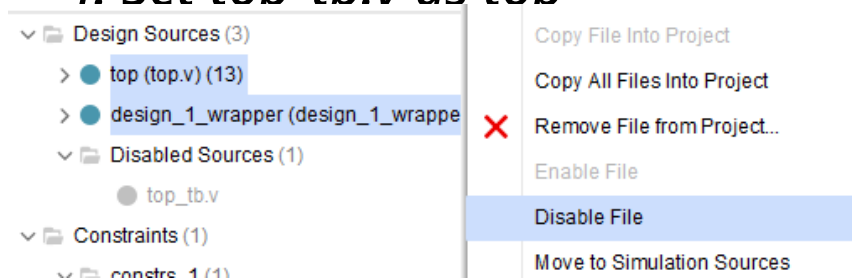1. Disable top.v
2. Disable design_1_wrapper.v
3. Enable top_tb.v
4. Set top_tb.v as top



FPFA synthesis

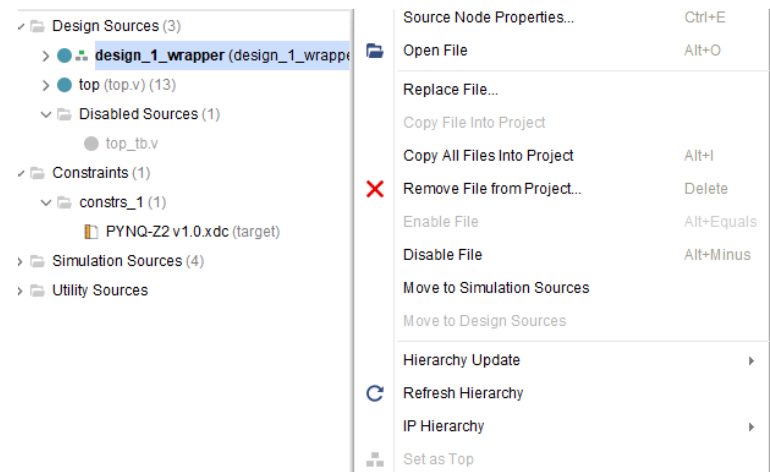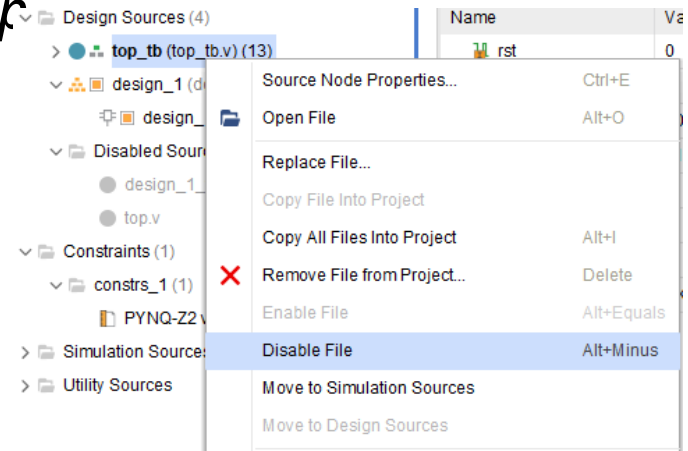
1. Enable top_tb.v
2. Enable top.v
3. Enable design_1_wrapper.v
4. Set design_1_wrapper.v as top



基礎題

產生一組clock divider之波型，結報需解釋波型的產生方法與波型圖擷圖(如下圖)。

以及開發版LED4及LED5之成果照片(白燈，及紅綠藍色燈)

 



加分題


請解釋 TOP.v 所呼叫的各函式之程式碼

越詳細分數越高


沒寫不扣分

FPGA(60%)

 同學需在lab9_Breathing_LED的專案內的top.v檔實作呼吸燈電路。同學可依需求修改top檔案內非port name的部分(切記不可修改top.v 的port name，不然會合成失敗)。接著合成Bitstream檔並燒入到FPGA內。



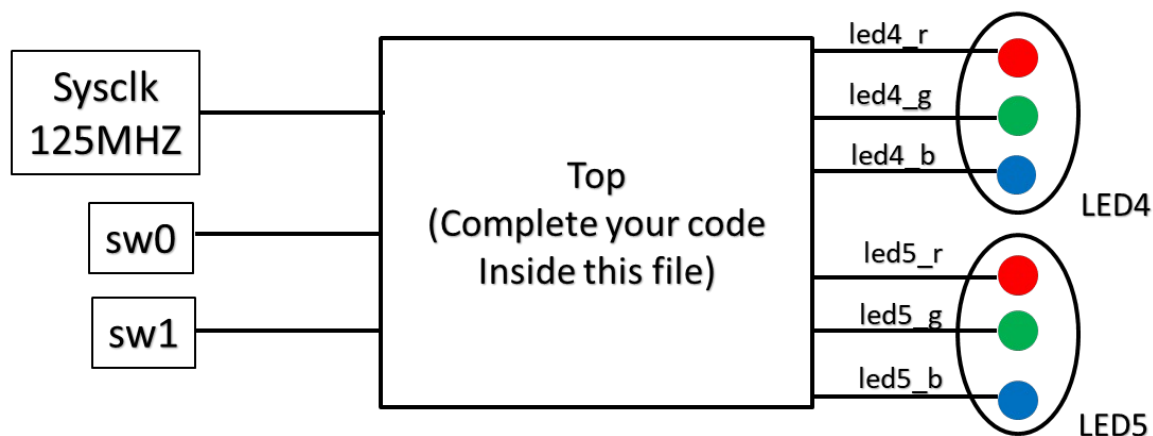- Note : FPGA內LED4、LED5內有三種獨立RGB LED燈。同學可自行挑選。沒有使用的output線路記得要在top module內接地。(Assign to 0)。




```
module top(  
    input sysclk,  
    input [1:0] sw,  
    input [3:0] btn,  
    output wire [3:0] led,  
    output wire led4_b,  
    output wire led4_g,  
    output wire led4_r,  
    output wire led5_b,  
    output wire led5_g,  
    output wire led5_r  
);
```


PYNQ-Z2 Board Hardware Introduction

PYNQ-Z2

Set Jumper to FPGA boot mode

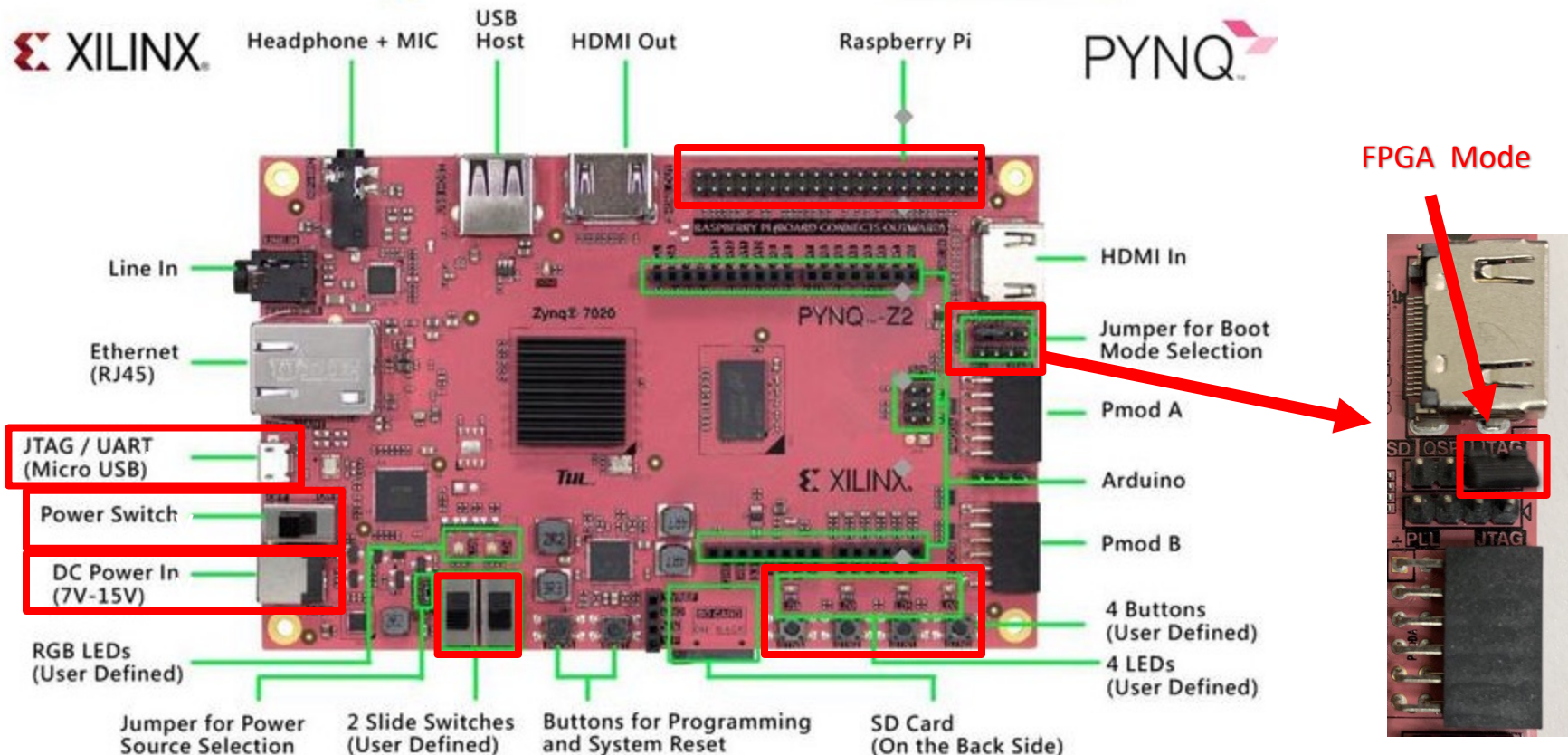



Install PYNQ-Z2 board file package

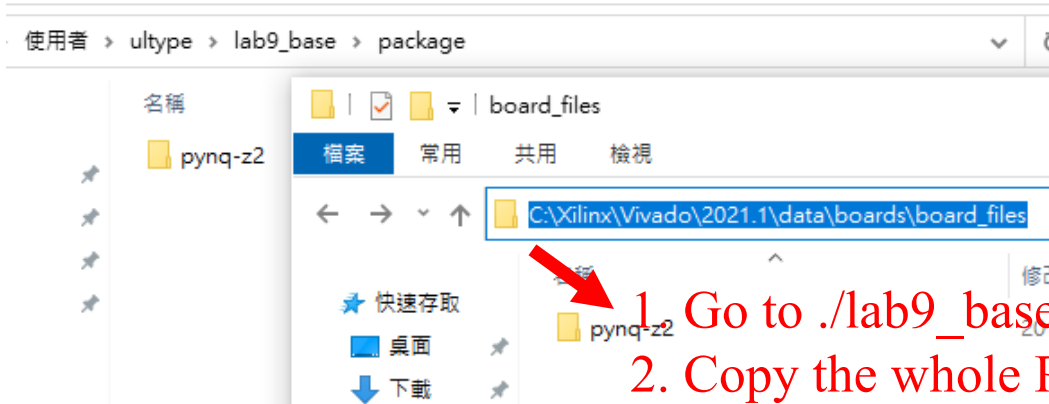

1. Go to `./lab9_base/package/`

 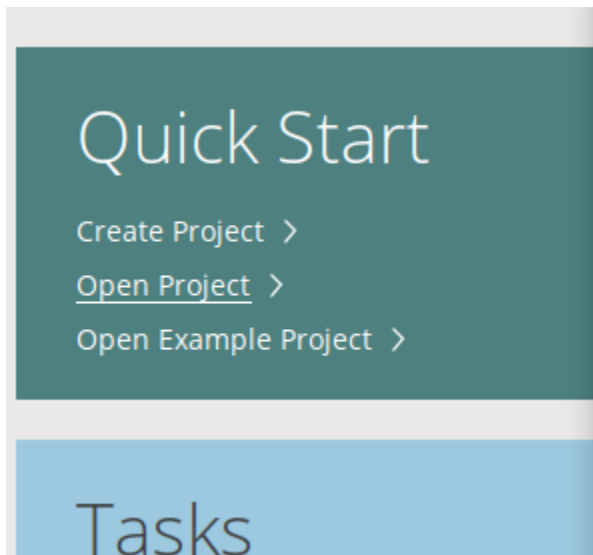2. Copy the whole PYNQ-Z2 folder to Vivado board files:

`PATH%/Xilinx/Vivado/2021.2/data/boards/board_files`





3. Open lab9 project template


Board Connection Checking

1. plug micro USB and power port
2. Turn on power switch
3. Connect to device
4. Check hardware panel


.Connect to device(Left down manual)

 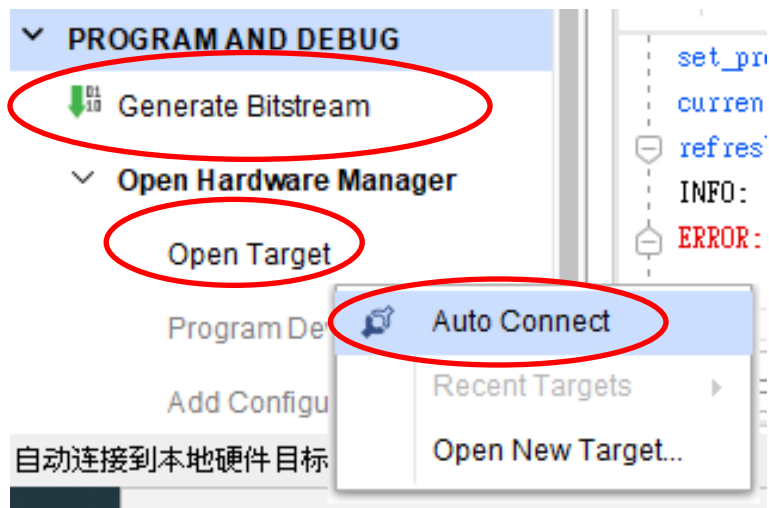

Hardware panel

 

FPGA 合成&燒錄

- 1  Run Synthesis
 > Open Synthesized Design
- 2  Run Implementation
 > Open Implemented Design
- 3  Generate Bitstream
 > Open Hardware Manager

Note up-right side

